

- 7 (a) Consider a circuit consisting of a resistor of resistance R , inductor of inductance L and a capacitor of capacitance C as shown in Figure 7. The capacitor is initially fully charged at time $t = 0$.

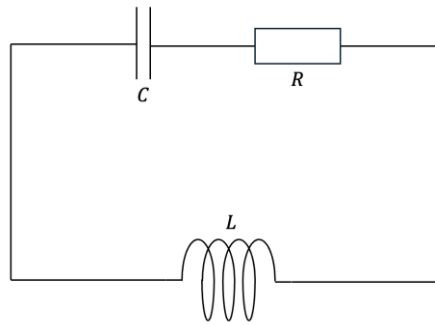


Figure 7

Given that the potential difference V in the capacitor is governed by the differential equation

$$\frac{d^2V}{dt^2} + \left(\frac{R}{L}\right)\frac{dV}{dt} + \left(\frac{1}{LC}\right)V = 0$$

Show that $V = Ae^{-\alpha t} \cos \omega t$ is a solution to the differential equation above where $\alpha = \frac{R}{2L}$. Hence, write down an equation for ω in terms of R , L and C . [5 marks]

Index no. _____

SPhO 2024 Theory Paper

- (b)(i) Given that $C = 15.0 \text{ nF}$, $L = 0.22 \text{ mH}$ and $R = 75.0 \Omega$, calculate the oscillation frequency of the circuit and the time taken for the amplitude of oscillation to decay to 10.0 % of its original value. [3 marks]

- (b)(ii) Calculate the value of R that would result in a critically damped circuit. [2 marks]