

4. In the figure shown, after the switch  $S$  is closed at time  $t = 0$ , the emf of the source is automatically adjusted to maintain a constant current  $I$  through  $S$ .
- (a) Find the current through the inductor as a function of time.  
[4 marks]
- (b) At what time is the current through the resistor equal to the current through the inductor?  
[1 mark]

