

Solutions for the 34th Singapore Physics Olympiad Theory Paper

1. Parallel-Plate Capacitor

This problem can be solved by modeling the capacitor as a combination of three separate capacitors.

- The left half of the device can be treated as a single capacitor, C_1 .
- The right half consists of two capacitors stacked vertically, in a **series** combination, C_2 and C_3 .
- The left half (C_1) and the right half (the series combination of C_2 and C_3) are in **parallel**.

The total capacitance C_{eq} is the sum of the capacitance of the left half and the equivalent capacitance of the right half (C_{23}).

$$C_{eq} = C_1 + C_{23}$$

where C_{23} is given by the formula for capacitors in series:

$$\frac{1}{C_{23}} = \frac{1}{C_2} + \frac{1}{C_3}$$

Step-by-step Calculation

1. **Calculate the capacitance of each section.** The formula for a parallel-plate capacitor is $C = \frac{\kappa\epsilon_0 A_{\text{plate}}}{d_{\text{separation}}}$.

- For C_1 : The area is $A/2$, the separation is $2d$, and the dielectric constant is κ_1 .

$$C_1 = \frac{\kappa_1\epsilon_0(A/2)}{2d} = \frac{\kappa_1\epsilon_0 A}{4d}$$

- For C_2 : The area is $A/2$, the separation is d , and the dielectric constant is κ_2 .

$$C_2 = \frac{\kappa_2\epsilon_0(A/2)}{d} = \frac{\kappa_2\epsilon_0 A}{2d}$$

- For C_3 : The area is $A/2$, the separation is d , and the dielectric constant is κ_3 .

$$C_3 = \frac{\kappa_3\epsilon_0(A/2)}{d} = \frac{\kappa_3\epsilon_0 A}{2d}$$

2. **Calculate the equivalent capacitance of the right half (C_{23}).** Since C_2 and C_3 are in series:

$$\begin{aligned}\frac{1}{C_{23}} &= \frac{1}{C_2} + \frac{1}{C_3} = \frac{2d}{\kappa_2\epsilon_0 A} + \frac{2d}{\kappa_3\epsilon_0 A} \\ &= \frac{2d}{\epsilon_0 A} \left(\frac{1}{\kappa_2} + \frac{1}{\kappa_3} \right) = \frac{2d}{\epsilon_0 A} \left(\frac{\kappa_3 + \kappa_2}{\kappa_2\kappa_3} \right) \\ C_{23} &= \frac{\epsilon_0 A}{2d} \left(\frac{\kappa_2\kappa_3}{\kappa_2 + \kappa_3} \right)\end{aligned}$$

3. **Calculate the total capacitance (C_{eq}).** Since C_1 and C_{23} are in parallel:

$$C_{eq} = C_1 + C_{23} = \frac{\kappa_1\epsilon_0 A}{4d} + \frac{\epsilon_0 A}{2d} \left(\frac{\kappa_2\kappa_3}{\kappa_2 + \kappa_3} \right)$$

We can factor out $\frac{\epsilon_0 A}{2d}$:

$$C_{eq} = \frac{\epsilon_0 A}{2d} \left(\frac{\kappa_1}{2} + \frac{\kappa_2\kappa_3}{\kappa_2 + \kappa_3} \right)$$

4. **Substitute the given values.** Given: $A = 10.5 \text{ cm}^2 = 10.5 \times 10^{-4} \text{ m}^2$, $2d = 7.12 \text{ mm} = 7.12 \times 10^{-3} \text{ m}$, $\kappa_1 = 21.0$, $\kappa_2 = 42.0$, $\kappa_3 = 58.0$, $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$.

$$\frac{\kappa_1}{2} = \frac{21.0}{2} = 10.5$$

$$\frac{\kappa_2 \kappa_3}{\kappa_2 + \kappa_3} = \frac{42.0 \times 58.0}{42.0 + 58.0} = \frac{2436}{100} = 24.36$$

$$\frac{\epsilon_0 A}{2d} = \frac{(8.85 \times 10^{-12})(10.5 \times 10^{-4})}{7.12 \times 10^{-3}} \approx 1.305 \times 10^{-12} \text{ F}$$

$$C_{eq} = (1.305 \times 10^{-12})(10.5 + 24.36) = (1.305 \times 10^{-12})(34.86)$$

$$C_{eq} \approx 4.55 \times 10^{-11} \text{ F} = 45.5 \text{ pF}$$